

Report
on
COEN 316 LABORATORY EXPERIMENT #5

**DATAPATH/CONTROL UNIT INTEGRATION AND SYSTEM
TESTING**

Submitted to

Hasiksishna Menon Thelakkal

Lab demonstrator's name

Date: December 5th, 2016
Due Date: December 6th, 2016

By

Michael Gravino

Name

27088140

student ID

Lab section: DI

Objectives

The objective of this laboratory is to design the CPU datapath and control unit and combine all previous labs to obtain a working CPU.

Theory

VHDL is used as a tool that allows the possibility to read the behavior of an electrical circuit that can be written by the user and it can also be converted to a physical component. It uses computers to design the digital circuits and it helps in the creation of more complex circuits as well

.

We also use Modelsim during this lab, it is a software that can simulate the HDL circuits you design with VHDL. It is used to test and debug the circuits mostly. We must also use the precision tool to get a schematic and the Xilinx software to obtain files needed for testing onto the hardware.

The control unit in this implementation is a combinational logic circuit whose inputs are the opcode and function fields of the instruction and the outputs are the 10 control signals. It will be used within the CPU's datapath when port mapping each component and ensure it correctly executes the code by pinpointing each function within his code.

Observations

In designing the datapath of this CPU I had to make a lot of components that the other 3 labs did not cover. When looking at the diagram of the CPU within the given lab manual I observed 3 mux's needed to be created, 1 sign extend block, 1 data cache, 1 instruction cache and 1 pc register. Once all remaining parts are created within VHDL, we can then start writing the CPU datapath. Within another VHDL file, we add all components to the cpu within the architecture of the CPU entity, this will be the final CPU once we port map all signals to their respective positions and with the newly created control unit, everything will work harmoniously. Here are the Instructions that I will be simulating within the modelsim results displayed shortly after:

```

addi    $rt0,$rs1,7          0010000000100000000000000000111 -> $rt0=7, $rs1=0
addi    $rt2,$rs1,6          00100000001000100000000000000110 -> $rt2=6, $rs1=0
sub     $rd3,$rt0,$rt2       000000000000000100001100000100010 -> $rd3=7-6=1,$rt0=7,$rt2=6
sw      $rt3,0($s5)          10101100101000110000000000000000 -> MM[0+$s5]=$rt3=1
and     $rt3,$rt3,$rt2       00000000011000100001100000100100 -> $rt3 = 1 AND 6 = 0
slti    $rt4,$rt3,2          00101000011001000000000000000010 -> $rt3=0 < imm=2, $rt4 = 1
lw      $rt6,0($s5)          10001100101001100000000000000000 -> $rt6 = MM[0+$s5]=1
or      $rt1,$rt6,$rt2 i_cache 00000000110000100000100000100101 -> $rt1 = 1 OR 6 = 7
xor     $rt5,$rt1,$rt2       000000000001000100010100000100110 -> $rt5 = 6 XOR 7 = 1
nor     $rt5,$rt5,$rt2       000000000101000100010100000100111 -> $rt5 = 0001 NOR 0006 = -8
andi    $rt3,$rt2,4          001100000100001100000000000000100 -> $rt3 = 6 ANDi 4 = 4
ori     $rt3,$rt5,7          001101001010001100000000000000111 -> $rt3 = -8 ORi 7 = -1
xori    $rt3,$rt3,6          001110000110001100000000000000110 -> $rt3 = -1 XORi 6 = -7
slt     $rt4,$rt5,$rt3       000000000101000110010000000101010 -> $rt4 = 1 --> -8 < -7
j       target              000010000000000000000000000010000 -> target = 10000
beq     $rt4,$rt6,1          000100001000011000000000000000001 -> if $rt4 == $rt6 then jump to ADD = 10001
bne     $rt5,$rt3,(FFFE)     000101001010001111111111111111110 -> if $rt5 != $rt3 then jump back to the previous instruction
bltz    $rt4,0               000001001000000000000000000000000 -> branch all the way back to address 00000 if $rt4 < 0
lui     $rt4,1               001111000000010000000000000000001 -> $rt4 = 1 << 16 = (65536)10
add     $rt4,$rt4,$rt4       000000000100001000010000000100000
jr      $rt10                00000001010000000000000000001000 -> jump to adress 00000 The whole program BEGINS executing again

```

This is the ModelSim depicting every case with regards to the instructions in the previous figure:

[illegible]

Here are the last 70 lines or so of the precision.log file:

```
# Info: [659]: Top module of the design is set to: datapath.
# Info: [657]: Current working directory: /nfs/home/m/m_gravin/Modelsim/FPGA_ADV/lab_impl_1.
# Info: [40000]: RTLC-Driver, Release RTLC-Precision 2016a.7
# Info: [40000]: Last compiled on Jun  2 2016 06:11:46
# Info: [44512]: Initialising...
# Info: [44504]: Partitioning design ....
# Info: [40000]: RTLCCompiler, Release RTLC-Precision 2016a.7
# Info: [40000]: Last compiled on Jun  2 2016 06:47:43
# Info: [44512]: Initialising...
# Info: [44522]: Root Module work.datapath(struct): Pre-processing...
# Info: [44506]: Module work.next_address(na_arch): Pre-processing...
# Info: [44506]: Module work.dff(behav): Pre-processing...
# Info: [44506]: Module work.i_cache(behav): Pre-processing...
# Info: [44506]: Module work.mux1(behav): Pre-processing...
# Info: [44506]: Module work.regfile(regfile_arch): Pre-processing...
# Info: [45251]: Built-in hardware memory core inferred for variable 't': regfile.reg1 depth = 32, width = 32'.
# Info: [44506]: Module work.sign_ex(behav): Pre-processing...
# Info: [44506]: Module work.mux2(behav): Pre-processing...
# Info: [44506]: Module work.alu(arch_alu): Pre-processing...
# Info: [44506]: Module work.d_cache(behav): Pre-processing...
# Info: [45251]: Built-in hardware memory core inferred for variable 't': d_cache.data_array depth = 32, width = 32'.
# Info: [44506]: Module work.mux3(behav): Pre-processing...
# Info: [44506]: Module work.control_unit(behav): Pre-processing...
# Info: [44508]: Module work.next_address(na_arch): Compiling...
# Info: [44508]: Module work.dff(behav): Compiling...
# Info: [44508]: Module work.i_cache(behav): Compiling...
# Info: [44508]: Module work.mux1(behav): Compiling...
# Info: [44508]: Module work.regfile(regfile_arch): Compiling...
# Info: [44508]: Module work.sign_ex(behav): Compiling...
# Info: [44508]: Module work.mux2(behav): Compiling...
# Info: [44508]: Module work.alu(arch_alu): Compiling...
# Info: [44508]: Module work.d_cache(behav): Compiling...
# Info: [44508]: Module work.mux3(behav): Compiling...
# Info: [44508]: Module work.control_unit(behav): Compiling...
# Info: [44522]: Root Module work.datapath(struct): Compiling...
# Info: [45205]: "/nfs/home/m/m_gravin/Modelsim/FPGA_ADV/.../Code/Lab5/next_address.vhd", line 36: Module work.next_address(na_arch), Net(s) next_pc[31:0]: Latch inferred.
# Info: [45205]: "/nfs/home/m/m_gravin/Modelsim/FPGA_ADV/.../Code/Lab5/alu.vhd", line 50: Module work.alu(arch_alu), Net(s) overflow: Latch inferred.
# Info: [45205]: "/nfs/home/m/m_gravin/Modelsim/FPGA_ADV/.../Code/Lab5/alu.vhd", line 51: Module work.alu(arch_alu), Net(s) zero: Latch inferred.
# Info: [45205]: "/nfs/home/m/m_gravin/Modelsim/FPGA_ADV/.../Code/Lab5/control_unit.vhd", line 34: Module work.control_unit(behav), Net(s) output_con[13:0]: Latch inferred.
# Info: [45205]: "/nfs/home/m/m_gravin/Modelsim/FPGA_ADV/.../Code/Lab5/control_unit.vhd", line 17: Module work.control_unit(behav), Net(s) control_unit[10]: Latch inferred.
# Info: [44846]: Rebalanced Expression Tree...
# Info: [44842]: Compilation successfully completed.
# Info: [44841]: Counter Inferencing === Detected : 1, Inferred (Modgen/Selcounter/AddSub) : 0 (0 / 0 / 0), AcrossDH (Merged/Not-Merged) : (0 / 0), Not-Inferred (Acrossdh/Attempted) : (0 / 0), Local Vars : 1 ===
# Info: [44856]: Total lines of RTL compiled: 500.
# Info: [44835]: Total CPU time for compilation: 0.0 secs.
# Info: [44513]: Overall running time for compilation: 5.0 secs.
# Info: [657]: Current working directory: /nfs/home/m/m_gravin/Modelsim/FPGA_ADV/lab_impl_1.
# Info: [15330]: Doing rtl optimisations.
# Info: [3022]: Reading file: /nfs/home/m/m_gravin/Modelsim/FPGA_ADV/.../Code/Lab5/labtest.ucf.
# Info: [657]: Current working directory: /nfs/home/m/m_gravin/Modelsim/FPGA_ADV/lab_impl_1.
# Info: [660]: Finished compiling design.
compile
# COMMAND: synthesise
# Info: [657]: Current working directory: /nfs/home/m/m_gravin/Modelsim/FPGA_ADV/lab_impl_1.
# Info: [4556]: 6 Instances are flattened in hierarchical block .work.datapath.struct.
# Info: [20013]: Precision will use 4 processor(s).
# Info: # [15002]: Optimising design view: work.regfile.regfile_arch_unfold_2862
# Info: # [15002]: Optimising design view: work.next_address.na_arch_unfold_2431
# Info: # [15002]: Optimising design view: work.d_cache.behav
# Info: # [15002]: Optimising design view: work.datapath.struct
# Info: # [15002]: Optimising design view: work.alu.arch_alu
# Info: # [15002]: Optimising design view: work.control_unit.behav_unfold_2325
# Info: [8048]: Added global buffer BUFGP for Port port:clk
# Info: [3027]: Writing file: /nfs/home/m/m_gravin/Modelsim/FPGA_ADV/lab_impl_1/datapath.edi.
# Info: [3027]: Writing file: /nfs/home/m/m_gravin/Modelsim/FPGA_ADV/lab_impl_1/datapath.ucf.
# Info: [657]: Current working directory: /nfs/home/m/m_gravin/Modelsim/FPGA_ADV/lab_impl_1.
# Info: [660]: Finished synthesising design.
# Info: [11019]: Total CPU time for synthesis: 2.2 s secs.
# Info: [11020]: Overall running time for synthesis: 4.0 s secs.
synthesise
# COMMAND: save_project
# Info: [9562]: Saved implementation lab_impl_1 in project /nfs/home/m/m_gravin/Modelsim/FPGA_ADV/lab.psp.
save_project
# COMMAND: close_project -discard
```

Here is the impact.log (last 30 lines or so):

```
----- GUI: Wizard Data Report -----
File Mode : ACECF
Collection Name : labtest
Collection Location : /nfs/home/m/m_gravin/Modelsim/Xilinx/
Collection Size : 0 Mbits
Reserved Space : 0 Mbits
Number of Design : 1
Config Address and Design Name list :
Version: 0 DesignName: rev0
----- END of Report -----
V2Pro Part: xc2vp30 w/2 ppc
// *** BATCH CMD : setMode -acecf
1. Initializing V2Pro File...
// *** BATCH CMD : addDevice -p 1 -file"/nfs/home/m/m_gravin/Modelsim/Xilinx/labtest/datapath.bit"
'1': Loading file '/nfs/home/m/m_gravin/Modelsim/Xilinx/labtest/datapath.bit'...
done.
INFO:IMPACT:1777 -
Reading /nfs/sw_cmc/x86_64.EL7/tools/xilinx_10.1/ISE/virtex2p/data/xc2vp30.bsd...
INFO:IMPACT:501 - '1': Added Device xc2vp30 successfully.
-----
Add one device.// *** BATCH CMD : setAttribute -configdevice -attr path -value"/nfs/home/m/m_gravin/Modelsim/Xilinx"
// *** BATCH CMD : generate -active labtest
INFO:IMPACT:794 - Creating SVF File /nfs/home/m/m_gravin/Modelsim/Xilinx/labtest/rev0/rev0.svf...

'1': Programming device...
PROGRESS_START - Starting Operation.
Match_cycle = NoWait.
Match cycle: NoWait
done.
INFO:IMPACT:579 - '1': Completed downloading bit file to device.
Match_cycle = NoWait.
Match cycle: NoWait
INFO:IMPACT - '1': Checking done pin....done.
'1': Programmed successfully.
PROGRESS_END - End Operation.
Elapsed time = 1 sec.
Creating Ace File /nfs/home/m/m_gravin/Modelsim/Xilinx/labtest/rev0/rev0.ace...
Copy active xilinx.sys /nfs/home/m/m_gravin/Modelsim/Xilinx/labtest/xilinx.systo root.
// *** BATCH CMD : saveProjectFile -file"/nfs/home/m/m_gravin/Modelsim/Xilinx/default.ipf"
```

And finally the listing of the working directory with the rev0.ace file:

```
[anole] [/home/m/m_gravin/Modelsim/Xilinx/lab5/rev0] > ls -al
total 1432
drwxrwx--- 2 m_gravin m_gravin 4096 Dec 6 08:36 .
drwxrwx--- 6 m_gravin m_gravin 4096 Dec 6 10:21 ..
-rw-rw---- 1 m_gravin m_gravin 1449758 Dec 6 08:36 rev0.ace
```

Conclusion

All in all this lab accomplished what it needed, I achieve the objectives that it set us out to complete. Because of this experiment I am more familiar using VHDL to design a CPU datapath as well as been reacquainted with the simulation software ModelSim and other related software to properly use it in the future. The hardest part of this lab was probably understanding what the lab manual wanted the CPU datapath to be and how exactly to implement it in an optimized and clear way without doing much debugging. This lab has helped me immensely with the material of this course and has bettered my understanding of CPUs and microprocessors and will definitely be of great help in my future endeavors.

Source Code

Control_Unit.vhd

```
library IEEE;
use IEEE.std_logic_1164.all;
use IEEE.std_logic_signed.all;

entity control_unit is
port(
    op_con: in std_logic_vector(5 downto 0);
    func_con: in std_logic_vector(5 downto 0);
    output_con : out std_logic_vector(13 downto 0)
);

end control_unit;

architecture behav of control_unit is
    signal control_unit1 : std_logic_vector(13 downto 0);
begin
    control_unit1 <=
        "11100000100000" when func_con = "100000"
    else
        "11101000100000" when func_con = "100010"
    else
        "10100000010000" when func_con = "101010"
    else
        "11101000110000" when func_con = "100100"
    else
        "11100001110000" when func_con = "100101"
    else
        "11100010110000" when func_con = "100110"
    else
        "11100011110000" when func_con = "100111"
    else
        "01111111000010" when func_con = "001000";

    output_con <=
        "10110000000000" when op_con = "001111"
    else
        "10110000100000" when op_con = "001000"
    else
        "10110000100000" when op_con = "001010"
    else
        "10110000110000" when op_con = "001100"
    else
        "10110001110000" when op_con = "001101"
    else
        "10110010110000" when op_con = "001110"
    else
        "10010010100000" when op_con = "100011"
    else
        "00010111100000" when op_con = "101011"
    else
        "01111111000001" when op_con = "000010"
    else
        "01111111001100" when op_con = "000001"
    else
        "00000000000100" when op_con = "000100"
    else
        "00000000001000" when op_con = "000101"
    else
        control_unit1 when op_con = "000000";
end behav;
```


Datapath.vhd

```
library ieee;
use ieee.std_logic_1164.all;
use ieee.std_logic_arith.all;
use ieee.std_logic_unsigned.all;

entity datapath is
port(
    reset : in std_logic;
    clk    : in std_logic;
    rs_out, rt_out : out std_logic_vector(3 downto 0); -- output ports from reg.file
    pc_out : out std_logic_vector(3 downto 0);
    overflow, zero : out std_logic
); -- will not be constrained in Xilinx since not enough LEDs
end datapath;

architecture struct of datapath is -- adding all components to the datapath

    component dff is -- component for the pc flip flop
    port (
        clk, reset: in std_logic;
        d : in std_logic_vector(31 downto 0);
        q: out std_logic_vector(31 downto 0)
    );
    end component;

    component i_cache is -- i-cache component
    port(
        in_add : in std_logic_vector(4 downto 0);
        output_cache: out std_logic_vector(31 downto 0)
    );
    end component;

    component d_cache is -- d-cache component
    port(
        clk, reset: std_logic;
        data_write: std_logic;
        add: std_logic_vector(4 downto 0);
        d_in: in std_logic_vector(31 downto 0);
        d_out: out std_logic_vector(31 downto 0)
    );
    end component;

    component mux1 is -- reg_dst mux component
    port (
        reg_dst: in std_logic;
        a: in std_logic_vector(4 downto 0);
        b: in std_logic_vector(4 downto 0);
        output_mux1: out std_logic_vector(4 downto 0)
    );
    end component;

    component mux2 is -- alu_src mux component
    port (
        alu_src: in std_logic;
        in1: in std_logic_vector(31 downto 0);
        in2: in std_logic_vector(31 downto 0);
        output_mux2: out std_logic_vector(31 downto 0)
    );
    end component;

    component mux3 is -- reg_in_src mux component
    port (
        reg_in_src: in std_logic;
        inp1: in std_logic_vector(31 downto 0);
        inp2: in std_logic_vector(31 downto 0);
```

```

        output_mux3: out std_logic_vector(31 downto 0)
    );
end component;

component sign_ex is -- sign extend component
port(
    func_sign: std_logic_vector(1 downto 0);
    inpt1: in std_logic_vector(15 downto 0);
    output_sign: out std_logic_vector(31 downto 0)
);
end component;

component regfile is -- register file component
port (
    din      : in std_logic_vector(31 downto 0);
    reset    : in std_logic;
    clk      : in std_logic;
    write    : in std_logic;
    read_a   : in std_logic_vector(4 downto 0);
    read_b   : in std_logic_vector(4 downto 0);
    write_address : in std_logic_vector(4 downto 0);
    out_a    : out std_logic_vector(31 downto 0);
    out_b    : out std_logic_vector(31 downto 0)
);
end component;

component alu is -- alu component
port (
    x, y : in std_logic_vector(31 downto 0);
    add_sub : in std_logic ;
    logic_func : in std_logic_vector(1 downto 0) ;
    func      : in std_logic_vector(1 downto 0) ;
    output    : out std_logic_vector(31 downto 0) ;
    overflow  : out std_logic ;
    zero      : out std_logic
);
end component;

component next_address is -- next address component
port(
    rt, rs: in std_logic_vector(31 downto 0); -- two register inputs
    pc: in std_logic_vector(31 downto 0);
    target_address: in std_logic_vector(25 downto 0);
    branch_type: in std_logic_vector(1 downto 0);
    pc_sel: in std_logic_vector(1 downto 0);
    next_pc: out std_logic_vector(31 downto 0)
);
end component;

component control_unit is -- control unit component
port(
    op_con: in std_logic_vector(5 downto 0);
    func_con: in std_logic_vector(5 downto 0);
    output_con : out std_logic_vector(13 downto 0)
);
end component;

-- all signals per the lab manuals diagram of the datapath

signal next_pc1, pc1, i_cacheout1, regfile_outa, regfile_outb, sign_ex1, mux2_out, alu1, d_cacheout1, mux3_out : std_logic_vector(31 downto 0);
signal output_control: std_logic_vector (13 downto 0);
signal mux1_out: std_logic_vector (4 downto 0);

begin

-- Port Mapping all ports of every component
Next_Address_Block: next_address port map
( rs => regfile_outa, rt => regfile_outb, pc => pc1, target_address => i_cacheout1(25 downto 0), branch_type => output_control(3 downto 2), pc_sel => output_control(1 downto 0), next_pc => next_pc1 );

PC_Block: dff port map
( clk => clk, reset => reset, d => next_pc1, q => pc1 );

I_Cache_Block: i_cache port map
( in_add => pc1(4 downto 0), output_cache => i_cacheout1 );

Mux1_Block: mux1 port map
( reg_dat => output_control(12), a => i_cacheout1(20 downto 16), b => i_cacheout1(15 downto 11), output_mux1 => mux1_out );

Register_File_Block: regfile port map
( din => mux3_out, reset => reset, clk => clk, write => output_control(13), read_a => i_cacheout1(25 downto 21), read_b => i_cacheout1(20 downto 16), write_address => mux1_out, out_a => regfile_outa, out_b => regfile_outb );

Sign_Extend_Block: sign_ex port map
( func_sign => output_control(8 downto 4), inpt1 => i_cacheout1(15 downto 0), output_sign => sign_ex1 );

Mux2_Block: mux2 port map
( alu_src => output_control(10), in1 => regfile_outb, in2 => sign_ex1, output_mux2 => mux2_out );

ALU_Block: alu port map
( x => regfile_outa, y => mux2_out, add_sub => output_control(9), logic_func => output_control(7 downto 6), func => output_control(5 downto 4), output => alu1, overflow => overflow, zero => zero );

D_Cache_Block: d_cache port map
( clk => clk, reset => reset, data_write => output_control(8), add => alu1(4 downto 0), d_in => regfile_outb, d_out => d_cacheout1 );

Mux3_Block: mux3 port map
( reg_in_src => output_control(11), in1 => d_cacheout1, in2 => alu1, output_mux3 => mux3_out );

Control_Unit_Block: control_unit port map
( op_con => i_cacheout1(31 downto 26), func_con => i_cacheout1(5 downto 0), output_con => output_control );

-- Outputs of CPU:
rs_out <= not (regfile_outa(3 downto 0));
rt_out <= not (regfile_outb(3 downto 0));
pc_out <= not (pc1(3 downto 0));

end struct;

```